

Amateur Bands: A Top to Ten TRF

Since the mid-1930's - because of its far superior selectivity - the super-heterodyne principle has been the de-facto standard for practically all radio receivers. In certain very specific situations, however, the simplicity and passiveness of the TRF has distinct advantages.

A **super-heterodyne** receiver contains an internal oscillator. This can introduce noise to the incoming signal and also cause the receiver to radiate a small signal, which could interfere with other equipment. A super-heterodyne is also vulnerable to strong "image" signals on the other side of the IFO (intermediate frequency off-set) oscillator. Weaker images can even occur at off-sets corresponding to multiples [or harmonics] of the IFO oscillator frequency.

There are also inherent tracking errors between the IFO oscillator and the received pass-band centre, which can effectively shift the resulting intermediate frequency, thereby attenuating signals differently at different parts of the tuning range. For higher frequencies, double conversion super-heterodynes are necessary, which can augment the tracking error and noise problems.


The use of an IF off-set beat-frequency oscillator [BFO], for hearing carrier-only Morse Code transmissions, introduces yet more noise and can generate spurious harmonics between the BFO and the IFO oscillator.

A **tuned radio frequency** [TRF] receiver, on the other hand, is entirely passive in operation. It does not, within itself, generate any radio-frequency signals. It is therefore much quieter [generates less spurious noise] than a super-heterodyne and tracking errors cannot exist. I have therefore opted for the much simpler TRF design. Selectivity and audio shaping will be done using a comprehensive audio filter placed between the receiver's audio output and the final audio amplifier.

A variable capacitor with a capacitance ratio 3:4 facilitates a frequency ratio [between the bottom of its tuning range and the top of its tuning range] of about 1.15. Consequently, the ratio between the *pass-band width* at the low end of its tuning range and the *pass-band width* at the high end of its tuning range is also 1.15. So, if the pass-band at the low end of its tuning range be 10 kHz wide, then the pass-band at the high end of its tuning range will be 11.5 kHz wide. A constant pass-band width, of up to 10 kHz, for the receiver, across the whole of its tuning range, can easily be determined by a subsequent audio filter.

With this regime, a straight-forward TRF receiver can be more than adequately selective for use on any of the amateur bands from Top to Ten. It renders the use of the super-heterodyne principle unnecessary.

A block diagram of the basic TRF receiver is shown below. The red line marks the boundary between what I call the Front End and what I call the Back End. The Front End deals with the RF signal up to its detection: the extraction of the audio content. The Back End deals with shaping and amplifying the audio content. I propose that there be a separate instance of the Front End for each of the Amateur Bands, which share, in turn, a single instance of the Back End. Different Front Ends may contain different numbers of RF stages to achieve necessary RF selectivity.

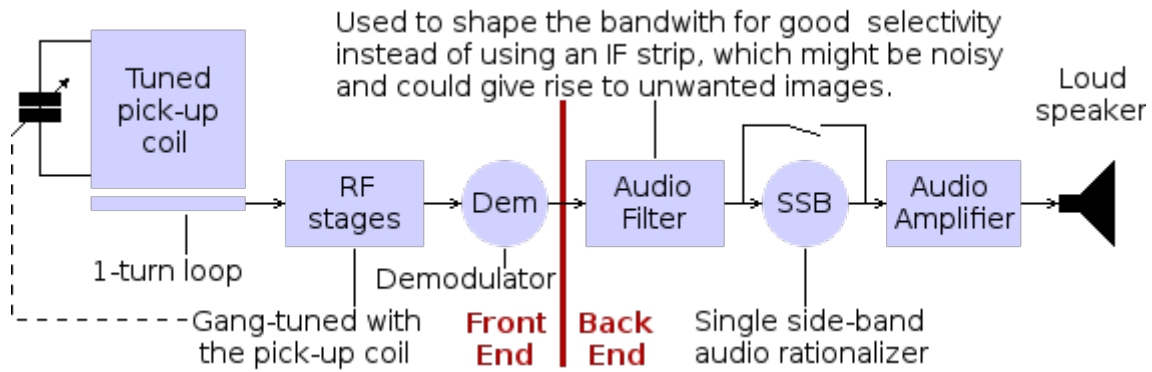

I first consider the Front End, beginning with my preferred design for the signal pick-up coil and RF stage tuning coils for each Amateur Bands from Top to Ten.

Pick-up and Tuning Coils

To provide a well-defined low-noise pass-band, I have opted not to use an aerial wire or any form of rod antenna to pick up the arriving signal. Instead, I have decided to use a very large and very high-Q coil to capture the magnetic vector of the arriving signal. The magnetic vector of the arriving signal is also less prone to artificially generated radio interference. This coil is to be tuned using a section of the multi-gang variable capacitor used to tune the radio-frequency stages of the receiver. The fact that the signal pick-up device is variably tuned means that a narrower lower-noise signal is supplied to the input of the receiver.

The pick-up coil should be mounted with its axis vertical. This will cause it to pick up signals that are horizontally polarized electrically, which is correct for practically all transmissions on these bands. It will have a good omni-directional horizontal gain. Its tuning capacitor should be mounted quite close to it, being varied via a tort cord and pulley system ganged to the receiver's tuning capacitors. Alternatively, the capacitor could be varied via a synchro motor linked to a synchro generator mounted on the receiver's main tuning shaft. The pick-up coil can be mounted inside a building but it should be mounted as high as practicable, away from steel-reinforced walls or beams.

The illustration on the right shows a mast-mounted version of a pick-up coil for Top Band [160 metres: 1695 to 1957 kHz]. The 10-metre mast is a hollow perspex tube 50mm diameter. It is kept vertical by three guys running 20° from the vertical and spaced 120° apart around the mast. Each guy is fixed to an anchor half-way up the mast. At this half-way point are three horizontal radials of 13mm perspex tube also spaced 120° apart but off-set from the guys by 60°. These act as spacers for three pole-guys, whose purpose is to keep the whole of the mast straight. The [top short cylinder](#) is the pick-up coil. The lower one houses the tuning control servo and feeder terminator.



The tuned circuits for the RF stages of the receiver use smaller coils with the same inductance as the pick-up coil. The parameters and dimensions for the pick-up and tuning coils for the HF Amateur Radio Bands are shown below.

These values were calculated using [Calculator 1](#), which opens in a separate tab. This **calculates** a coil's inductance, the top frequency of the desired tuning range, the coil's radius, its number of turns, its diameter [=length] and the amount of wire required **from** the minimum frequency of the tuning range, the maximum and minimum of the variable capacitor and the desired coil pitch. The length and diameter of the coil are made equal because, in practice, this results in the highest Q-factor [inductor with minimum inherent capacitance]. Alternatively, **if** you prefer to specify the coil's diameter [=length], pitch and tuning range, **then** use [Calculator 2](#), which also opens in a separate tab.

For best results, all coils should be wound with Litzwire, which comprises a number of separately insulated strands of fine copper or silver wire plaited into a light composite cable.

Coils For The Amateur Top Band: 1695 to 1957 kHz

Frequency ratio: 1.154572271

Use tuning capacitor range 375 to 500 pF

Minimum frequency, F_{min} = 1695 kHz

Inductance needed to tune 1695000 Hz with 500 pF capacitance:

$L = 0.000017633188645396083$ Henries.

Maximum frequency attainable with 375 pF capacitor:

$F_{max} = 1957217.4125528312$ Hertz

Pick-up Coil

Make the pitch, $P = 0.02$ metres per turn.

Coil radius, $R = 0.1090777629951081$ metres

Coil winding, $N = 10.90777629951081$ turns

Length=diameter, $D = 0.2181555259902162$ metres

Wire required, $W = 7.47889015033212$ metres

Tuning Coil

Make the pitch, $P = 0.005$ metres per turn

Coil radius, $R = 0.04328753893119314$ metres

Coil winding, $N = 17.31501557247725$ turns

Length=diameter, $D = 0.1175004582538685$ metres

Wire required, $W = 4.71019647271448$ metres

Coils For The 80-Metre Amateur Band: 3.5 to 4.0 MHz

Frequency ratio: 1.142857143

Use a 90 to 120 pF 3-gang variable capacitor.

Minimum frequency, F_{min} = 3.5 kHz

Inductance needed to tune F_{min} with 120 pF capacitance:

$L = 0.00001723149381222418$ Henries.

Maximum frequency attainable with 90 pF capacitor:

$F_{max} = 4041451.8843273805$ Hertz

Pick-up Coil

Make the pitch, $P = 0.02$ metres per turn.

Coil radius, $R = 0.1082431064691129$ metres

Coil winding, $N = 10.82431064691129$ turns
Length=diameter, $D = 0.2164862129382258$ metres
Wire required, $W = 7.364920521041236$ metres

Tuning Coil

Make the pitch, $P = 0.005$ metres per turn.
Coil radius, $R = 0.04295630526934391$ metres
Coil winding, $N = 17.18252210773756$ turns
Length=diameter, $D = 0.08591261053868782$ metres
Wire required, $W = 4.63840011078122$ metres

It picks up the signal's magnetic vector, so it can be placed inside a brick building provided the walls contain no magnetic materials (iron, nickel or cobalt).

Coils For The 40-Metre Amateur Band: 6.5 to 7.5 kHz

Frequency ratio: 1.153846154

Use a 27 to 36 pF 3-gang variable capacitor.
Minimum frequency, $F_{min} = 6.5$ kHz
Inductance needed to tune F_{min} with 36 pF capacitance:
 $L = 0.00001665371196842179$ Henries.
Maximum frequency attainable with 27 pF capacitor:
 $F_{max} = 7505553.499465135$ Hertz

Pick-up Coil

Make the pitch, $P = 0.02$ metres per turn.
Coil radius, $R = 0.10701950908942125$ metres
Coil winding, $N = 10.701950908942123$ turns
Length=diameter, $D = 0.2140390181788425$ metres
Wire required, $W = 7.199424688850118$ metres

Tuning Coil

Make the pitch, $P = 0.005$ metres per turn.
Coil radius, $R = 0.08834265830642155$ metres
Coil winding, $N = 35.33706332256862$ turns
Length=diameter, $D = 0.1766853166128431$ metres
Wire required, $W = 22.47302633266358$ metres

Coils For The 20-Metre Amateur Band: 13 to 15 MHz

Frequency ratio: 1.153846154

Use a 7.5 to 10 pF 3-gang variable capacitor.
Minimum frequency, $F_{min} = 13$ MHz
Inductance needed to tune 13 MHz with 7.5 pF capacitance:
 $L = 0.000014988340771579611$ Henries.
Maximum frequency attainable with 10 pF capacitor:
 $F_{max} = 15011106.99893027$ Hertz

Pick-up Coil

Make the pitch, $P = 0.02$ metres per turn.
 Coil radius, $R = 0.14023522872928076$ metres
 Coil winding, $N = 14.023522872928075$ turns
 Length=diameter, $D = 0.28047045745856153$ metres
 Wire required, $W = 10.053125844402867$ metres

Tuning Coil

Make the pitch, $P = 0.005$ metres per turn.
 Coil radius, $R = 0.04100502963267555$ metres
 Coil winding, $N = 16.402011853070217$ turns
 Length=diameter, $D = 0.0820100592653511$ metres
 Wire required, $W = 4.2266461138243665$ metres

The axis of the aerial coil is vertical, so the polarization of the aerial is horizontal, which is normal for this band.

Coils For The 15-Metre Amateur Band: 20 to 23 MHz

Frequency ratio: 1.15

Use a 3 to 4 pF 3-gang variable capacitor.
 Minimum frequency, $F_{min} = 20$ MHz
 Inductance needed to tune 20 MHz with 4 pF capacitance:
 $L = 0.000015831434939980964$ Henries.
 Maximum frequency attainable with 3 pF capacitor:
 $F_{max} = 23094010.767585028$ Hertz [23 MHz]

Pick-up Coil

Make the pitch, $P = 0.02$ metres per turn.
 Coil radius, $R = 0.10522833489277751$ metres
 Coil winding, $N = 10.522833489277751$ turns
 Length=diameter = 0.21045666978555502 metres
 Wire required, $W = 6.960555010955296$ metres

Tuning Coil

Make the pitch, $P = 0.005$ metres per turn.
 Coil radius, $R = 0.041759892376414254$ metres
 Coil winding, $N = 16.7039569505657$ turns
 Length=diameter = 0.08351978475282851 metres
 Wire required, $W = 4.38366582298374$ metres

Coils For The 10-Metre Amateur Band: 27.5 to 30.5 MHz

Frequency ratio: 1.109090909

Use a 2 to 2.5 pF 3-gang variable capacitor.
 Minimum frequency, $F_{min} = 28$ MHz
 Inductance needed to tune F_{min} with 2.5 pF capacitance:
 $L = 0.000013397842461603724$ Henries.

Maximum frequency attainable with 2 pF capacitor:
 $F_{max} = 30745934 \cdot 690622106$ Hertz [30.7 MHz]

Pick-up Coil

Make the pitch, $P = 0.02$ metres per turn.
 Coil radius, $R = 0.08510026246010823$ metres
 Coil winding, $N = 8.510026246010822$ turns
 Length = Diameter = 0.17020052492021645 metres
 Wire required, $W = 4.553499137014897$ metres

Tuning Coil


Make the pitch, $P = 0.005$ metres per turn.
 Coil radius, $R = 0.03377206153798642$ metres
 Coil winding, $N = 13.508824615194564$ turns
 Length = Diameter = 0.06754412307597284 metres
 Wire required, $W = 2.867315845231706$ metres

The axis of the aerial coil is vertical, so the polarization of the aerial is horizontal, which is normal for this band.

I have omitted the 30, 17 and 12 metre Amateur Bands because these were allocated much later and are not so well used. You can use my calculators to calculate the specifications of the coils required for these bands if you wish. The minimum to maximum frequency ratio of the short-wave broadcast bands is of the same order as those of the amateur bands. The same TRF technique can therefore be successfully employed for receiving broadcasts from around the world on these bands too. Coils for the short-wave broadcast bands can also be specified using my coil calculators.

The Front End


A more detailed schematic of the Front End is shown below. Each RF resonator (pick-up or tuning coil with its respective variable capacitor) is electrically isolated. It is coupled only *inductively* to the rest of the receiver. In the case of the pick-up coil, the signal is picked up from the resonator by a single turn of Litz wire wound on one end of the coil former. Each tuning coil has a loop comprising a few turns of wire wound at each end of the main resonator coil. One loop is to allow the input signal to energize the resonator. The other is to pick up the output signal from the resonator.

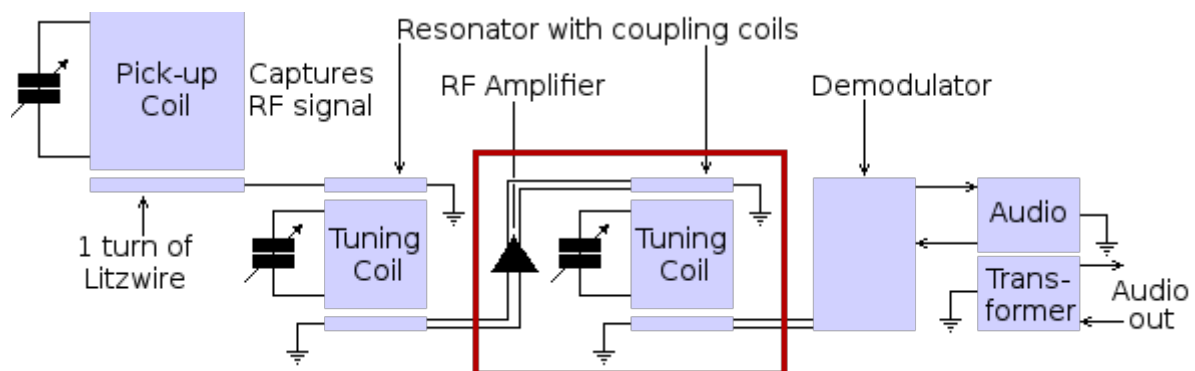

An RF amplifier then strengthens the signal and passes it to the next resonator. I have shown only two resonator stages. More can be added as required to achieve the desired pass-band width at the

low-frequency end of the tuning range. Resonator stages are added by repeating the detail within the red rectangle above. The resonators of the different stages can be off-set one side or the other of the pick-up resonator's frequency in order to flatten the top of the pass-band profile. The final resonator feeds the signal to the demodulator.

The demodulator extracts the audio frequency content of the original RF signal. The RF signal is taken from the final RF resonator via a small inductive coupling coil comprising a few turns of Litz wire wound at one end. The coupling coil is earthed at its mid point to provide a balanced source. Opposing diodes separate the +ve and -ve halves of the RF signal. Their outputs are fed to the balanced input of an audio transformer with a centre-tapped primary. The inductance of the audio transformer's primary winding is well high enough to block the RF components of the signal, thus allowing only the audio content to pass through to the output winding.

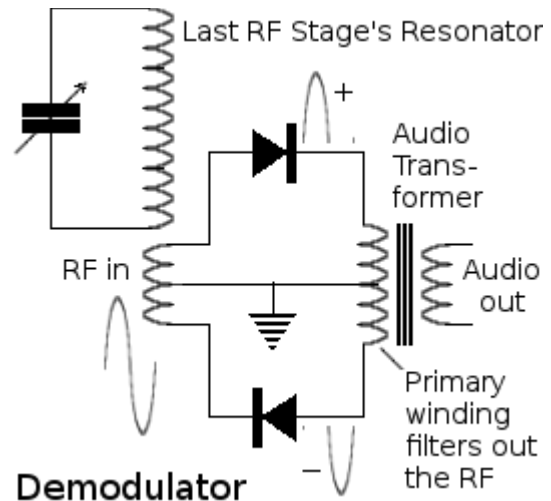


I prefer the centre-tapped transformer configuration with just two diodes because this allows both the radio and audio frequency signals to be balanced with respect to chassis potential (earth or ground). Impedance calculations should take account that each half-cycle at radio frequency uses only half of the radio frequency coupling coil's winding and that likewise, each half-cycle at audio frequency uses only half of the primary winding of the audio transformer. I also prefer to earth (ground) the centre tap of the audio transformer output winding to balance the audio signal with respect to chassis, thus minimizing its susceptibility to electrical interference on its way to the receiver's Back End, which is in a separate cabinet.


If amplification is necessary at this stage, the opposing diodes could be replaced by op-amps configured for +ve and -ve inputs and outputs respectively. Forming a Morse Code tone from a keyed continuous wave transmission or reconstituting the speech from a single-sideband transmission is done later in the Back End of the receiver. I think it must be nostalgia that makes me yearn to implement the RF amplifiers herein using electro-thermionic triodes. Notwithstanding, I think I will always end up using packaged op-amps.

The Back End

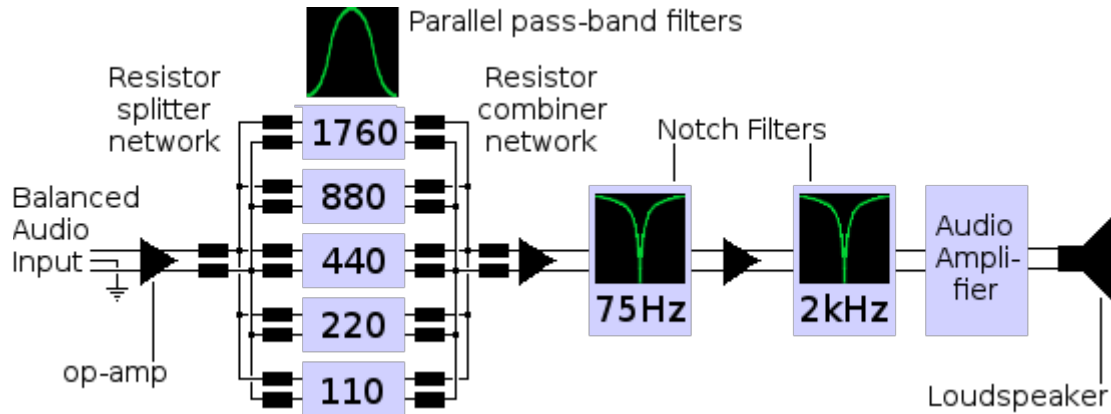There is a separate Front End for each radio band. These all share just one Back End. A block schematic of the Back End is shown below.





The Back End receives, from the Front End to which it is currently connected, a balanced audio signal. Because of the 1:1.15 frequency ratio of the Front End's pass-band between the lower and upper ends of its tuning range, the pass-band of the audio signal presented to the Back End will vary by the same factor of 1:1.15. The function of the Back End is firstly to make the audio pass-band constant over the whole tuning range. It achieves this objective by allowing only 5 octaves of the audio spectrum to pass through to the audio amplifier and loudspeaker. The highest unattenuated frequency allowed through is thus 16 times the lowest unattenuated frequency allowed through. Each of the 5 permitted octaves is allowed to pass through its own one-octave wide tuned filter. This requires 5 different and separate one-octave filters wired in parallel, as shown in the diagram above.

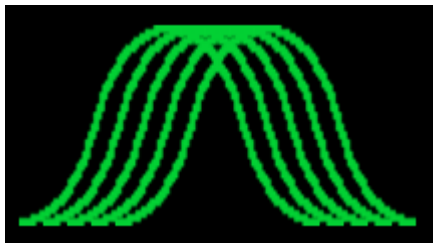

The centre frequencies chosen for the 5 parallel acceptance filters are 110, 220, 440, 880 and 1760 Hertz. The trace on the left shows the 5 overlapping acceptance bands peaked one octave apart. The horizontal axis shows frequency according to a logarithmic scale. The vertical axis shows the amplitude of the signal allowed through.

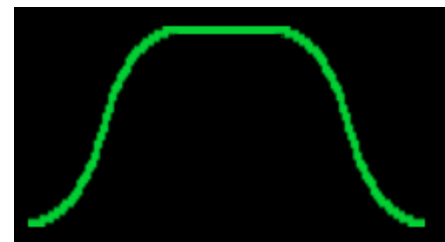
The pass-band profile produced by combining the outputs of the 5 acceptance filters is shown on the right. This now has the correct 5-octave bandwidth. However, its sides are not yet sufficiently steep. In other words, the degree to which it rejects all frequencies above and below the desired pass-band is not yet adequate.



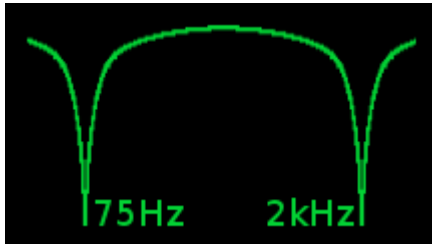

For this reason, the signal, gained by merging the outputs of the 5 parallel acceptance filters, is amplified and then passed through two successive rejection (or notch) filters. Each of these strongly rejects signals at frequencies at - and close to - its tuning point (75Hz and 2kHz respectively), as shown in the trace on the left.

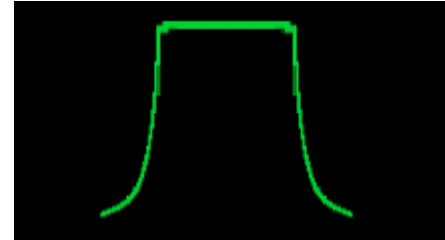
This causes a steep attenuation of the audio signal at the upper and lower boundaries of the desired 5-octave frequency range. The resulting pass-band now approximates much more closely to the ideal square all-or nothing profile, as shown on the right. The output signal from the second notch filter is then passed on to a good quality audio amplifier.



The Acceptance Filters

I have decided to use 5 inductance-capacitance filters whose centre frequencies correspond to the A-note in each of 5 octaves of the piano. Middle-A on the piano has a frequency of 440 hertz. Each A-note going down the keyboard has half the frequency of the previous A-note. Each A-note going up the keyboard has double the frequency of the previous A-note. The centre frequencies for my 5 pass-band filters are therefore 110, 220, **440**, 880, 1760 hertz.

A diagram of an LC (inductance-capacitance) pass-band filter is shown on the right. The inductive reactance of the coil, $X_L = 2\pi fL$, where f is the frequency of the presented signal and L is the value of its inductor in *henries*. The capacitive reactance of the capacitor, $X_C = 1/(2\pi fC)$, where C is the value of the capacitor in *farads*. The filter passes the incoming signal with least opposition when $X_C = X_L$.

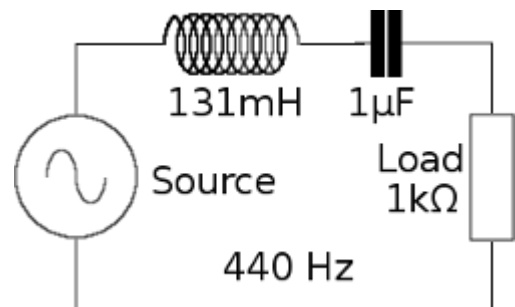

The following calculator calculates the required inductance value in henries for a pass-band filter of a given centre-frequency and standard capacitor value. Type in your values for frequency and capacitance and press the carriage-return key within either of these fields. The required inductance appears in the third (bottom) field. The default values shown are for a filter which will allow through signals that fall within the octave centred on Middle-A [440 Hz].

Pass-band Frequency, F_{min}	<input type="text"/>	Hertz
Chosen Capacitance, C_{max}	<input type="text"/>	Farads
Required Inductance, L	<input type="text"/>	Henries

Hertz	Farads	Henries
110	0.0000100	0.209
220	0.0000100	0.052
440	0.0000010	0.131
880	0.0000010	0.033
1760	0.0000001	0.082


The table on the left shows the values thus calculated for the 5 filters I need to limit my audio pass-band to frequencies which fall only within the 5 octaves I require. However, the calculations have given some awkward values for the inductances required. I would like to see how far the centre frequencies of my filters will be perturbed if I use the nearest standard inductor values.

The following calculator takes the standard capacitor value from the previous calculator and calculates the filter's centre frequency from an entered inductor value. So, if I use a 130 millihenry inductor instead of the 130.8383053310797 millihenry inductor value given by the first calculator, I get a centre-frequency value of 441.4163908290642 hertz instead of 440 hertz. I can live with that.

Adjusted Inductance, L	<input type="text"/>	Henries
Centre Frequency, F_{min}	<input type="text"/>	Hertz


The table on the right gives the centre-frequencies of my 5 filters where I am using more rounded values for the inductances. Of these, the worst is only about 4% out, which is somewhere in between the notes A and A#. I don't think that this could make any perceptible difference to the range of frequencies which will ultimately arrive at the listener's ears.

Farads	Henries	Hertz
0.0000100	0.200	113
0.0000100	0.050	225
0.0000010	0.130	441
0.0000010	0.030	919
0.0000001	0.080	1779

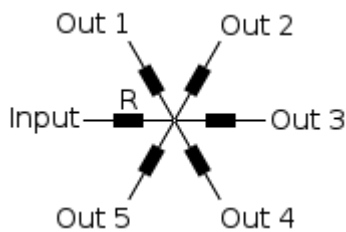


Each of the 5 pass-band filters must pass its respective octave of the audio signal. This necessitates that the 5 pass-band filters must operate in parallel. The output from the Back End's first op-amp must therefore be split 5 ways to provide a separate independent input for each filter. This splitting is done by what is, in effect, a 6-way star network of resistors, as shown on the left.

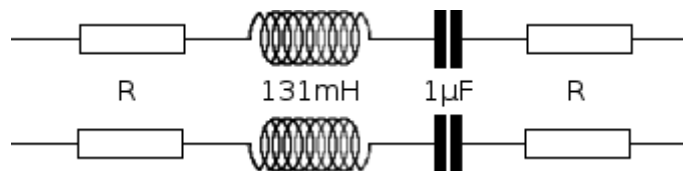The 6 ways comprise one input and 5 outputs. The value, R, of each resistor must be one sixth the operating impedance of the op-amp and the filters. There must be a separate 5-way splitter for each of the two outputs from the balanced op-amp. Each pass-band filter thus comprises two identical instances of the following circuit.




The values shown are for the 440 Hz filter. The four resistors, R, all have the same value in all filters, equal to one sixth of the impedance of the op-amp's outputs. The two resistors on the left are each part of a separate 6-way star splitter. The two resistors on the right are each part of a separate 6-way star signal merger, which merges the outputs of the 5 pass-band filters ready for input to the Back End's second op-amp. Ideally, I would include an op-amp in each filter, as show below.

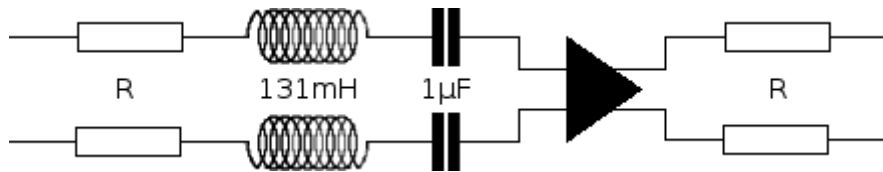

I would make the gain of the op-amp manually adjustable by means of a sliding variable resistor. This would allow me to even out any irregularity in the pass-band and also reduce the bandwidth in the presence of troublesome higher octave interference.


Notch Filters

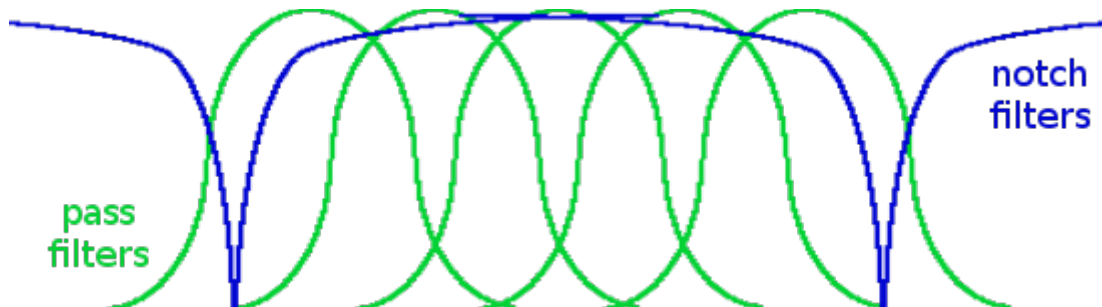The upper and lower edges of the composite pass-band of the 5 filters so far described are not steep enough to completely avoid interference on frequencies just outside the pass-band. I shall therefore steepen these edges by placing notch rejection filters, one either side of the pass-band, as shown in the following graph.




All these signals should add up to a reasonably steep-sided rectangular pass-band.

A circuit diagram of the generic LC (inductance-capacitance) rejection (or notch) filter is shown on the right. The relationship between resonant frequency, capacitance and inductance is the same as for an acceptance (or pass-band) filter. The same calculators, as before, can therefore be used also to calculate the values of the components (inductor and capacitor) required for the Back End's rejection filters.

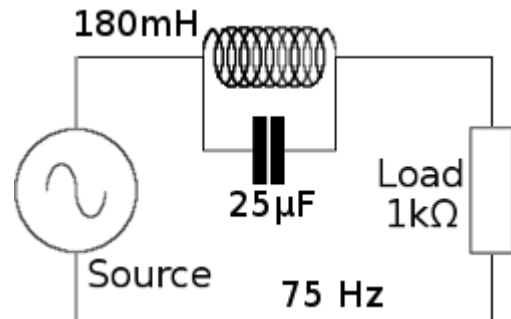

Recap: The coil's inductive reactance, $X_L = 2\pi fL$, where f is the frequency of the presented signal and L is the coil's inductance in *henries*. The capacitor's capacitive reactance, $X_C = 1/(2\pi fC)$, where C is its capacitance in *farads*. The filter rejects the incoming signal with maximum opposition when $X_C = X_L$. The values shown in the above diagram are for a 75Hz rejection filter. This rejects (does not allow to pass through) signals with frequencies at and around 75 Hz.

The two rejection (notch) filter stages of the Back End are shown in the following diagram. These stages form a balanced two-channel system, using two-channel differential op-amps. One channel carries the positive half-cycles of the audio signal while the other channel carries the negative half-cycles of the audio signal. Since there are two stages with two channels, four notch filters are required, each shown in a red square. Thus there are two 75Hz filters and two 2kHz filters.

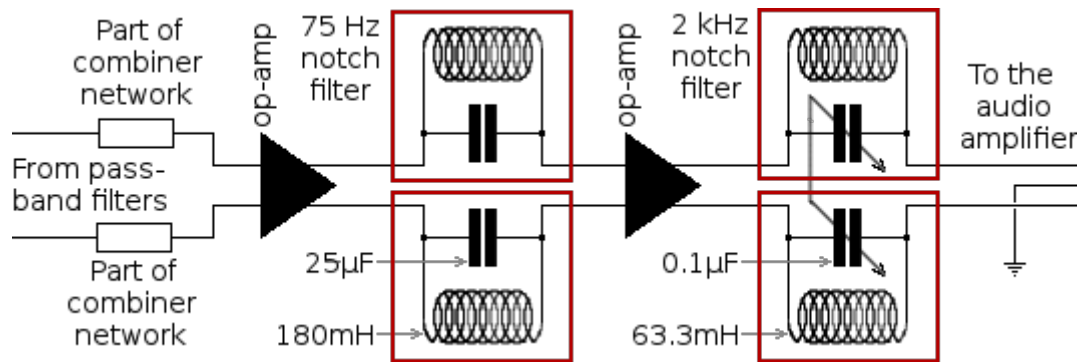

I have used variable capacitors in the 2kHz notch filters. These variable capacitors are ganged. This allows me to move the notch frequency in case I need to eliminate a troublesome heterodyne on any particular frequency. The 0.1µF capacitance can be made up, in practice, of a lower value variable capacitor with an additional fixed capacitor.

The output from the second notch filter is passed - via a balanced feed - to a good quality audio amplifier and loudspeaker.

Useful References

<http://www.allaboutcircuits.com/textbook/alternating-current/chpt-8/resonant-filters/>

<http://coil32.net/ferrite-toroid-core.html>

<http://electronics.stackexchange.com/questions/103435/naively-mixing-two-or-perhaps-more-audio-signals>

<http://www.circuitstoday.com/3-channel-audio-splitter>

©13 Sept to 05 Oct 2016 Robert John Morton

© The content of this document file is free and may be reproduced unmodified in its entirety, including all headers and footers, or as “fair usage” quotations that are attributed as follows: “ - [article name] by Robert John Morton <http://robmorton.20m.com/>”